



DC-DC BOOST CONVERTOR
For
Mini Project – 1A
(REV- 2019 'C' Scheme) of Second Year (Semester-
III) Bachelors in Engineering

By

Prathamkumar Bumb D9B 07

Pritam Dhamak D9B 13

Aadarsh Dubey D9B 16

Swaraj Muraskar D9B 32

Supervisor

Mrs. Manisha Joshi



Department of Electronics and Telecommunication

Vivekanand Education Society's Institute of

Technology Mumbai University

2022-2023

Mini Project-1A Approval

Project entitled by **DC-DC Boost Convertor** is approved for the Second year of Engineering.

Examiners

1. _____
2. _____

Supervisors

1. _____
2. _____

Date:

Place:

Certificate

This is to certify that **Prathamkumar Bumb, Pritam Dhamak, Aadarsh Dubey and Swaraj Muraskar** have completed the project report on the topic **DC-DC Boost Convertor** satisfactorily in partial fulfillment of the requirements for the award of Mini Project 1A (REV- 2019 'C' Scheme) of Second Year, (Semester-III) in Electronics and Telecommunication under the guidance **Mrs. Manisha Joshi** of during the year 2022-2023 as prescribed by University of Mumbai.

Supervisor

Head of Department
Dr. Chandansingh Rawat

Principal
Mrs. Jayalekshmi Nair

Examiner 1

Examiner 2

Declaration

We declare that this written submission represents our ideas in our words and where others' ideas or words have been included, we have adequately cited and referenced the original sources. We also declare that we have adhered to all principles of academic honesty and integrity and have not misinterpreted or fabricated or falsified any idea/data/fact/source in my submission. We understand that any violation of the above will be cause for disciplinary action by the Institute and can also evoke penal action from the sources which have thus not been properly cited or from whom proper permission has not been taken when needed.

Prathamkumar Bumb

Pritam Dhamak

Aadarsh Dubey

Swaraj Muraskar

Date:

Table of Contents

Chapter No.	Title	Page no.
	List of figures	i
	List of tables	ii
	Abstract	1
Chapter 1:	Introduction	2
Chapter 2:	Literature Review	3
	2.1 Survey	
	2.2 Research Gap	
Chapter 3:	Project Description	5
	3.1 Problem Definition	
	3.2 Steps Involved	
	3.3 Block Diagram	
	3.4 Component Description	
	3.4.1 Components Used	
	3.4.2 Components Description	
	3.5 Working of the project	
	3.6 Calculation	
Chapter 4:	Implementation	14
	4.1 Hardware	
	4.3 Software	
	4.3 Flowchart	
Chapter 5:	Result	18
Chapter 6:	Conclusion	21
	References	22
	Datasheets	23

List of Figures

Figure No.	Title	Page No.
Fig. 3.3.1	Block diagram of general DC-DC boost convertor	5
Fig. 3.4.1	IC 555 pinout	7
Fig. 3.4.2	Pinout of 1000uf capacitor	7
Fig. 3.4.3	Symbol of 1nf capacitor	8
Fig. 3.4.4	Pinout of Mosfet	8
Fig. 3.4.5	Actual photo of Schottky Diode(STPS2045C)	9
Fig. 3.4.6	Potentiometer	9
Fig. 3.4.7	Coiled Inductor	10
Fig. 3.4.8.	LM7805 Pinout	10
Fig. 3.5.1	Closed switch mode	11
Fig. 3.5.2	Open switch mode	12
Fig. 4.1.1	Implementation on GPB	15
Fig. 4.1.2	Implementation on PCB	15
Fig. 4.2.1	Top View Of PCB	16
Fig. 4.2.2	Bottom View Of PCB	16
Fig. 4.3.1	Flowchart of working	17
Fig. 4.3.2	Flowchart of process	17
Fig. 5.1	Proteus simulation	18
Fig. 5.2	Output waveform of first IC 555	19
Fig. 5.3	Output waveform of second IC 555	19
Fig. 5.4	Result on GPB	19
Fig. 5.5	Final result on PCB	20

List of Table

Table No.	Title	Page No.
Table 3.4.1	Components used	6
Table 3.6.1	Calculations	13

Abstract

The switching mode power supply market is flourishing quickly in today's world. Design engineers aren't always supplied with the desired amount of voltage they need in order to make their design function properly. Adding an extra voltage supply to a design is not always cost efficient. This is proposed to provide the designer with a method of boosting DC voltage , by using a boost converter designed specifically for this task. By using boost converters not only the cost for making the circuits is reduced, the circuit will be more proficient by using the DC DC boost converters. All aims, calculations, tests, data and conclusions have been documented within this report.

Chapter 2

Introduction

Power for the boost converter can come from any suitable DC sources, such as DC generators, batteries, solar panels and rectifiers. The method that changes one DC voltage to a different DC voltage is called DC to DC conversion. Generally, a boost converter is a DC to DC converter with an output voltage greater than the source voltage. It is sometimes called a step-up converter since it “steps up” the source voltage.

In many technical applications, it is required to convert a set voltage DC source into a variable-voltage DC output. A DC-DC switching converter converts voltage directly from DC to DC and is simply known as a DC Converter. A DC converter is equivalent to an AC transformer with a continuously variable turns ratio. It can be used to step down or step up a DC voltage source, as a transformer. DC converters are widely used for traction motor control in electric automobiles, trolley cars, marine hoists, forklifts trucks, and mine haulers. They provide high efficiency, good acceleration control and fast dynamic response. They can be used in regenerative braking of DC motors to return energy back into the supply. This attribute results in energy savings for transportation systems with frequent stops. DC converters are used in DC voltage regulators; and also are used, with an inductor in conjunction, to generate a DC current source, specifically for the current source inverter.

Chapter 2

Review of Literature

2.1 Literature Survey

Paper 1,

Title: A DC–DC multilevel boost converter [1]

Authors: Rosas-Caro JC, Ramirez JM, Peng FZ, Valderrabano A.

Year of publication: 2010

Methodology: A DC–DC converter topology is proposed.

Results: It is proposed to be used as DC link in applications where several controlled voltage levels are wanted with self balancing and unidirectional current flow.

Drawbacks: Unidirectional current, each device blocks only one voltage level.

Paper 2,

Title: A non isolated multiinput multioutput DC–DC boost converter for electric vehicle applications [2]

Authors: Nahavandi A, Hagh MT, Sharifian MB, Danyali S.

Year of publication: 2014

Methodology: A new non isolated multiinput multioutput dc-dc boost converter is proposed in this paper

Results: This converter is applicable in hybridizing alternative energy sources in electric vehicles.

Drawbacks: Low-voltage gains without extremely low duty cycles

2.1 Research Gap

1.In reference to the first paper, it is on a multilevel converter which has multiple outputs and the conversion rises from 50V to 300V. Whereas, on the other hand, our proposed converter is bound to work in a range which is compatible with the low-voltage devices[1].

2..In reference to the second paper mentions a multi input-multi output converter which has outputs with different dc voltage levels, the conversion rate it showed was very low as it went from 35V to 40V and 80V, even though the accessories they used were much more advanced and outnumbered our model[2].

Thus, we have created a model which is not only cost efficient but also provides a similar conversion efficiency to the papers mentioned above.

Chapter 3

Project Description

This chapter briefly describes the problem statement , steps involved while doing the project and the whole working of the project.

3.1 Problem Statement

Circuits powered by batteries, such as laptops and mobile phones. All of these electronic devices mostly have many sub-circuits, and all of that requires a certain voltage level other than that supplied by the battery. The voltage of the battery will reduce as its stored energy is nearly depleted, keeping it from outputting a constant voltage level. Multiple control voltage can be generated from a single battery voltage and this method was offered by DC to DC converters without using multiple batteries for different components of the equipment.

3.2 Steps involved

Steps followed for the implementation of DC-DC BOOST CONVERTORS using IC 555 are given below:

1. A circuit diagram was first created and analyzed for the given problem statement.
2. Simulation of this circuit diagram was made and run using PROTEUS software.
3. Faults in this circuit diagram were identified and addressed accordingly based on the simulation results.
4. The given circuit diagram was implemented on a breadboard and temporary connections between the components were made.
5. Power supply was given to the circuit and the results were noted.
6. PCB design of the circuit was made using EAGLE software.
7. PCB was fabricated and all the components were mounted and the circuit was implemented on a PCB.

3.3 Block Diagram of proposed Project

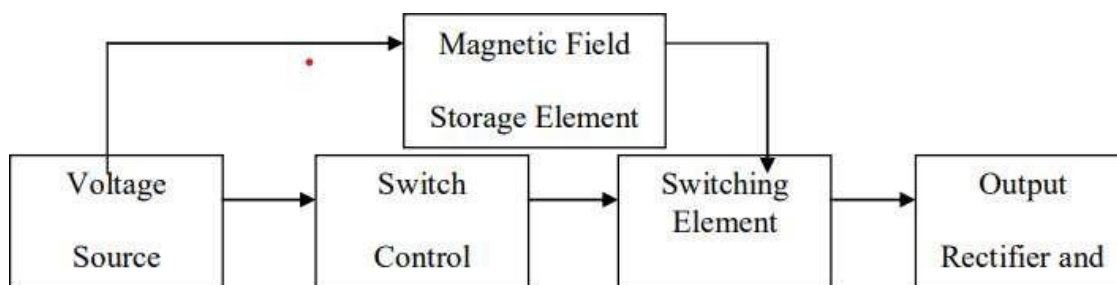


Fig. 3.3.1 Block diagram of general DC-DC boost convertor

The voltage source provides the input DC voltage to the switch control, and also to the magnetic field storage element. The block which contains switch control directs the action of the switching element, whereas the output rectifier and filter deliver an acceptable DC voltage to the output.

- Voltage Source - Input DC voltage source to power on the circuit (6V To 12V DC)
- Switching Element - Mosfet used to short circuit the inductor to the gnd to (sudden change in current build up it magnetic field)
- Magnetic Field Storage Element - Inductor is used as Magnetic Field Storage Element
- Switch Control - NE555
- Output & Rectifier - Diode is used dump the voltage change across inductor into output capacitor (for setting up the output v)

3.4 Component Description:

3.4.1. Components Used:

Table 3.4.1 Components Used

Sr. No.	Name of Components	Specification	Quantity
1	Integrated circuit	IC 555	2
2	Capacitor	1000uF	1
3	Capacitors	1nF	2
4	Mosfet	IRF540N or NCE8295A	1
5	Potentiometer	10k	1
6	Diode	STPS2045C	1
7	Inductor	52uH	1
8	Resistors	47k Ω , 1k Ω , 10k Ω , 22 Ω	1,2,5,1
9	Capacitors	100nF	4
10	Capacitor	470uF	1
11	Voltage Regulator	LM7805	1
12	Comparator	LM358A	1

3.4.2 Description of Components

3.4.2.1 IC 555:

IC 555 timer is a one of the most widely used IC in electronics and is used in various electronic circuits for its robust and stable properties. It works as a square-waveform generator with duty cycle varying from 50% to 100%, Oscillator and can also provide time delay in circuits. The 555 timer got its name from the three 5k ohm resistors connected in a voltage-divider pattern which is shown in the figure below. A simplified diagram of the internal circuit is given below for better understanding as the full internal circuit consists of over more than 16 resistors, 20 transistors, 2 diodes, a flip-flop and many other circuit components.


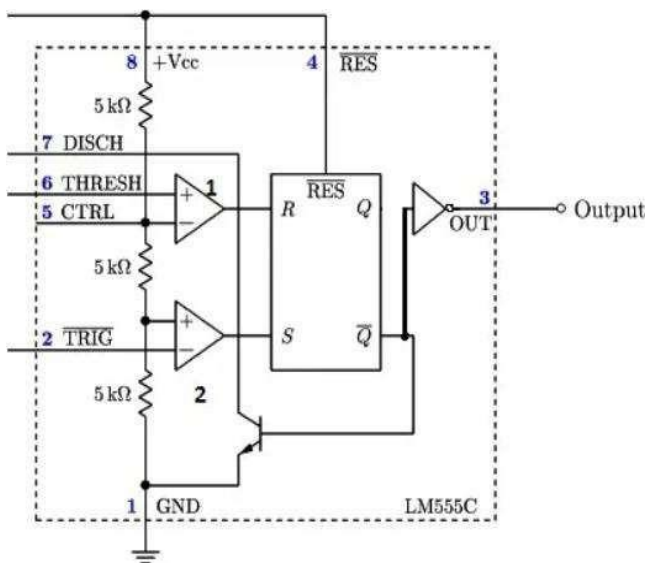


Fig. 3.4.1 IC 555 pinout

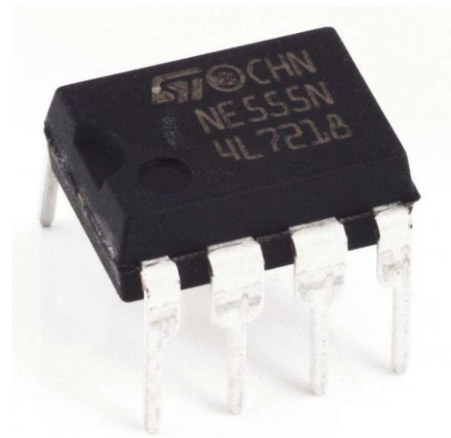

3.4.2.2 Capacitor:

A] 100uf:

This **1000uF 50V** capacitor is a good quality radial polarized Electrolytic capacitor. Electrolytic capacitors are widely used in switched-mode power supplies, **DC-DC** converters, and power supplies. This capacitor has a long life, low leakage current, and wide operating range.



Fig. 3.4.2 Pinout of 1000uf capacitor

B] Ceramic Capacitor:

A ceramic capacitor is a fixed-value capacitor where the ceramic material acts as the dielectric. It is constructed of two or more alternating layers of ceramic and a metal layer acting as the electrodes. The composition of the ceramic material defines the electrical behavior and therefore applications.

Specifications:

- Capacitance 1000pF
- Tolerance(%) ± 10
- Voltage (V) 50
- Operating Temperature Range -55°C to 125°C
- Mounting Type :Through Hole



Fig. 3.4.3 Symbol of 1nf capacitor

3.4.2.3 Mosfet:

The working principle of MOSFET is very simple and it includes three terminals namely source, drain and gate . Once we apply the signal at the transistor's Gate terminal, then both the terminals like drain and gate will be shorted. Whenever the Drain and the Gate gets shorted, then only we can get the preferred results, or else it will generate unnecessary outputs.

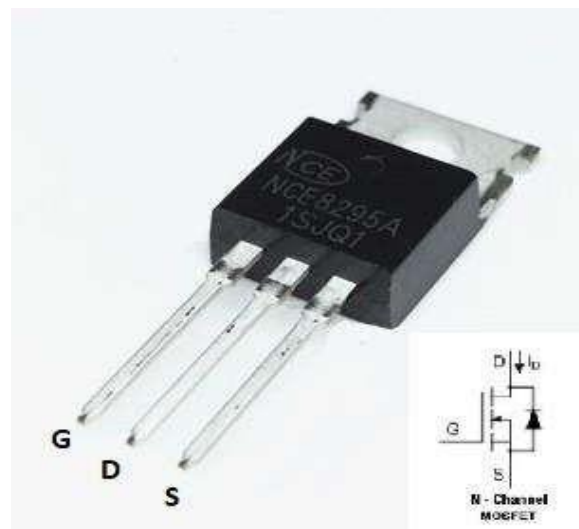


Fig. 3.4.4 Pinout of Mosfet

3.4.2.4 Schottky Diode(STPS2045C):

Dual center tap Schottky rectifier suited for switch mode power supply and high frequency DC to DC converters. Packaged either in TO-220AB, TO-220FPAB, or D²PAK, this device is especially intended for use in low voltage, high frequency inverters, free wheeling and polarity protection applications

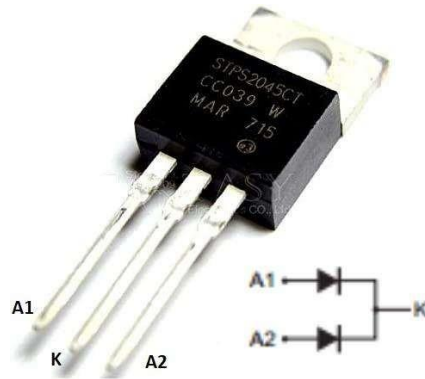


Fig. 3.4.5 Actual photo of Schottky Diode(STPS2045C)

3.4.2.5 Potentiometer:

A potentiometer (also known as a pot or potmeter) is defined as a 3 terminal variable resistor in which the resistance is manually varied to control the flow of electric current. A potentiometer acts as an adjustable voltage divider. A potentiometer is a passive electronic component. Potentiometers work by varying the position of a sliding contact across a uniform resistance. In a potentiometer, the entire input voltage is applied across the whole length of the resistor, and the output voltage is the voltage drop between the fixed and sliding contact. Fig 3.5 Potentiometer. Potentiometer is use to vary the duty cycle, to keep the the output voltage constant.

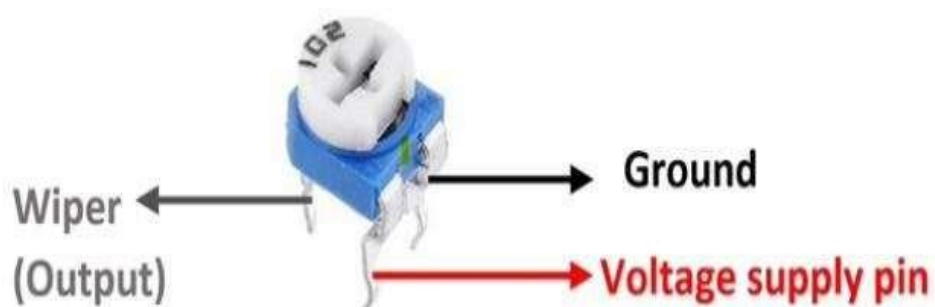


Fig. 3.4.6. Potentiometer

3.4.2.6 Inductor:

An inductor is a coil of wire that stores energy in the form of a magnetic field. The magnetic field depends on current flowing to "store energy."

If the current stops, the magnetic field collapses and creates a spark in the device that is opening the circuit.



Fig. 3.4.7. Coiled Inductor

3.4.2.7 LM7805:

The LM340 and LM7805 Family monolithic 3-terminal positive voltage regulators employ internal current limiting, thermal shutdown and safe-area compensation, making them essentially indestructible. If adequate heat sinking is provided, they can deliver over 1.5-A output current. They are intended as fixed voltage regulators in a wide range of applications including local (on-card) regulation for elimination of noise and distribution problems associated with single-point regulation. In addition to use as fixed voltage regulators, these devices can be used with external components to obtain adjustable output voltages and currents.

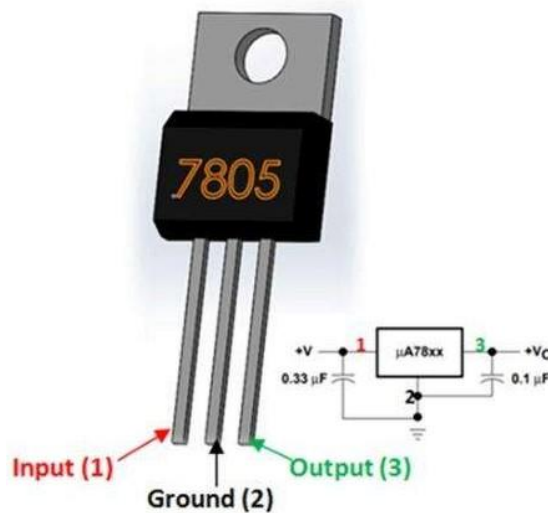


Fig.3.4.8. LM7805 Pinout

3.5 Working of proposed project

The boost converter is used to increase the output voltage by reducing the current, this is achieved by storing energy in an inductor and since the energy in an inductor cannot change instantly therefore, it starts storing the energy in its magnetic field. Current across the inductor is given by $V = L di/dt$. An inductor is connected in series with the voltage source to constantly turn on and off a circuit. A switch is connected in parallel to the voltage source and inductor for achieving fast switching we utilize a MOSFET along with a MOSFET driver. The circuit is connected to a load and a capacitor in parallel to it. In order to stop the current flowing backwards from the capacitor, a diode is used between the capacitor and the MOSFET.

The inductor tries to resist change in the current to provide a constant input current and hence the Boost converter acts as a constant current input source, while the load acts as the constant voltage source. The N-channel MOSFET is controlled by a PWM signal, we have used IC 555 timer to provide the output to the MOSFET. The capacitor is used to store the charge and provide a constant output to the load. The circuit works in 2 stages, in the 1st stage, the switch is turned on and in the 2nd stage, the switch is in the off stage.

Stage 1: Switch is on: Charging mode

In this condition the MOSFET switch is turned on. The MOSFET we have used is a N-channel IRFZ44N MOSFET, with its gate pin connected to the pin 3 of the IC555 timer. When the switch is in ON state, it completes the circuit across the inductor and the voltage is applied across it which results in a magnetic field around it. Since it offers a very low resistance path, all the voltage flows through the switch and goes back to the supply as marked by the red line in the figure below.

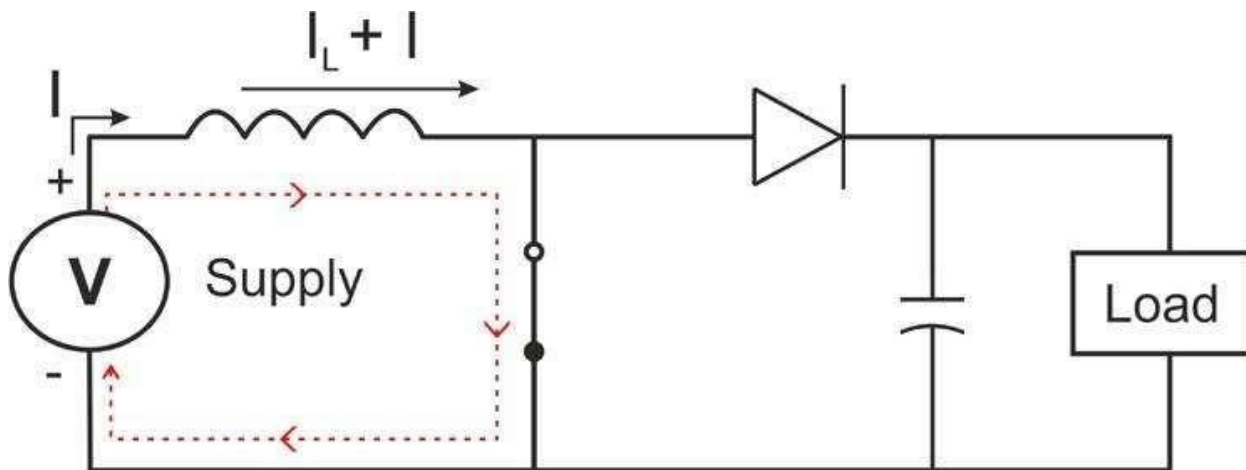


Fig 3.5.1 Closed switch mode

The capacitor which was previously charged during the last on stage tries to discharge itself from the MOSFET and to stop it, we use a diode in order to stop the charge from capacitor flowing in the reverse direction.

Stage 2: Switch is off: Discharging mode

When the switch is in the off state, the inductor's charging path is not completed, hence the polarity of the inductor is reversed and the magnetic field around it collapses as a result a voltage surge is generated which passes through the diode and charges the capacitor. The cumulative energy from the inductor and source is used to charge the capacitor as well as runs across the load.

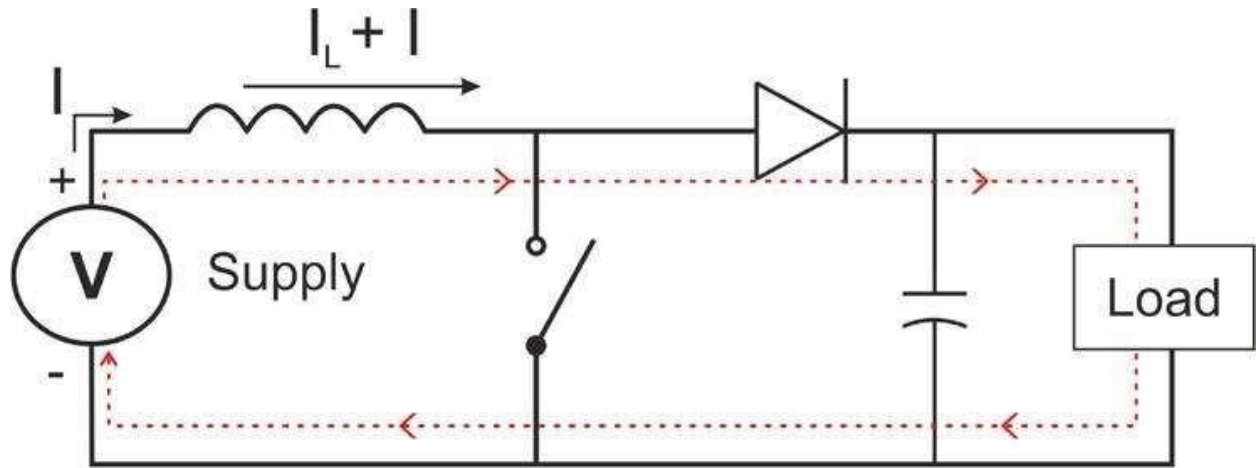


Fig 3.5.2 Open switch mode

3.6 Calculations

Table 3.6.1 Calculations

load	= 40Ω
Input voltage without load	= 12.1V
Input voltage with Load	= 11.9V
Output voltage without load	= 30.3V
Output voltage with load	= 29.71V
Input current without load	= 0.117A
Input current with load	= 2.063A
Output current with load	= 0.71A
Input power	= Input Voltage(with load) \times Input current(with load) = $11.9\text{V} \times 2.063\text{A}$ = 24.54 W
Output power	= Output current(with load) \times Output Voltage(with load) = $29.71\text{V} \times 0.71\text{A}$ = 21.094 W
Efficiency%	= $\frac{\text{Output Power}}{\text{Input Power}} \times 100$ = $\frac{21.094}{24.54} \times 100$ = 85.95%

Chapter 4

Implementation

4.1 Hardware:

This section describes the pinout of the both the IC's and the mosfet:

For IC 555(1st):

The IC is connected in the circuit as follows:

- Pin 1 of the IC is connected to the ground.
- Pin 2 and 6 of the IC are connected to the 1nf capacitor.
- Pin 3 which is output pin is connected to 2nd and 4th pin of second IC which is input to the second IC.
- Pin 7 is connected to resistors.
- Pin 8 is connected to the Vcc(input voltage).

For IC 555(2nd):

The second is connected in the circuit as follows:

- Pin 1 of the IC is connected to the ground.
- Pin 6 and 7 of the IC are connected to the 1nf capacitor.
- Pin 3 is connected to the gate of the mosfet and the resistor of 10k Ω .
- Pin 5 of the IC is connected to the output of the LM358.
- Pin 8 is connected to the Vcc(input voltage).

For Mosfet:

The mosfet is connected in the circuit as follows:

- Gate of Mosfet is connected to the output of the second IC.
- Drain of the Mosfet is connected to the inductor.
- Source of the Mosfet is grounded.

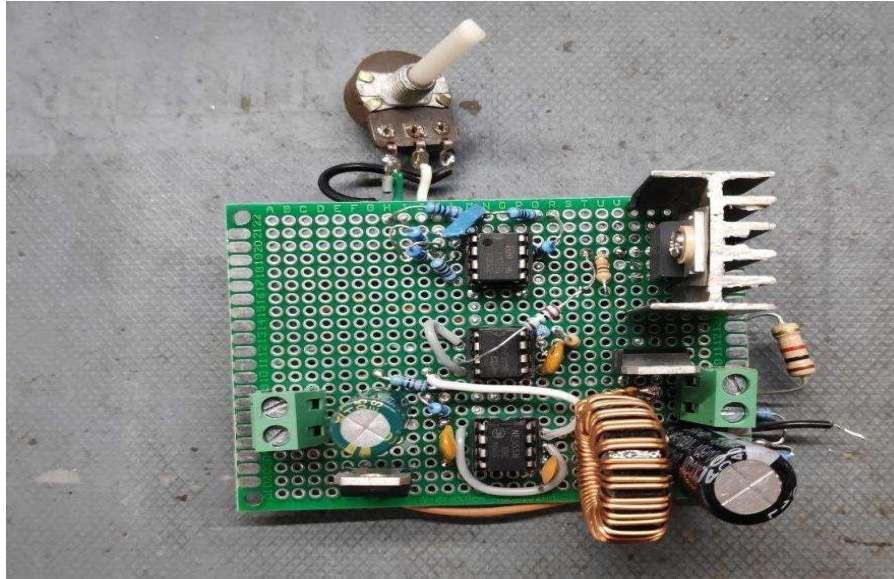


Fig. 4.1.1 Implementation on GPB

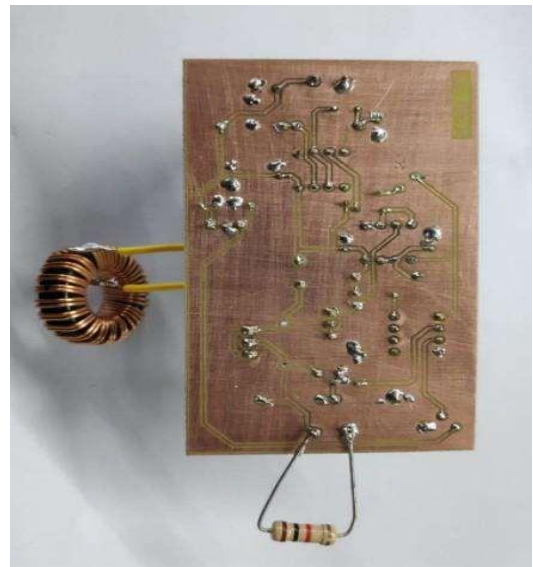
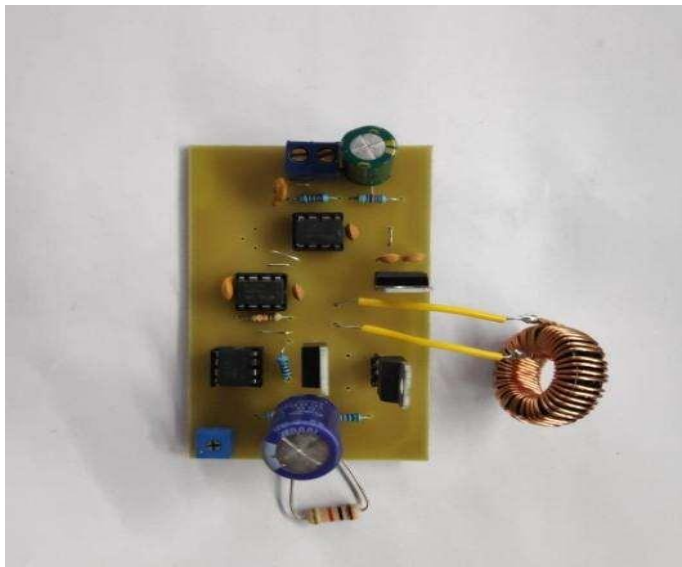


Fig. 4.1.2 Implementation on PCB

4.2 Software:

The PCB design of the above circuit was made using EAGLE software. Firstly, a circuit layout was made on the Eagle software and then this circuit layout was converted to a board file which was then printed in order to make the PCB.

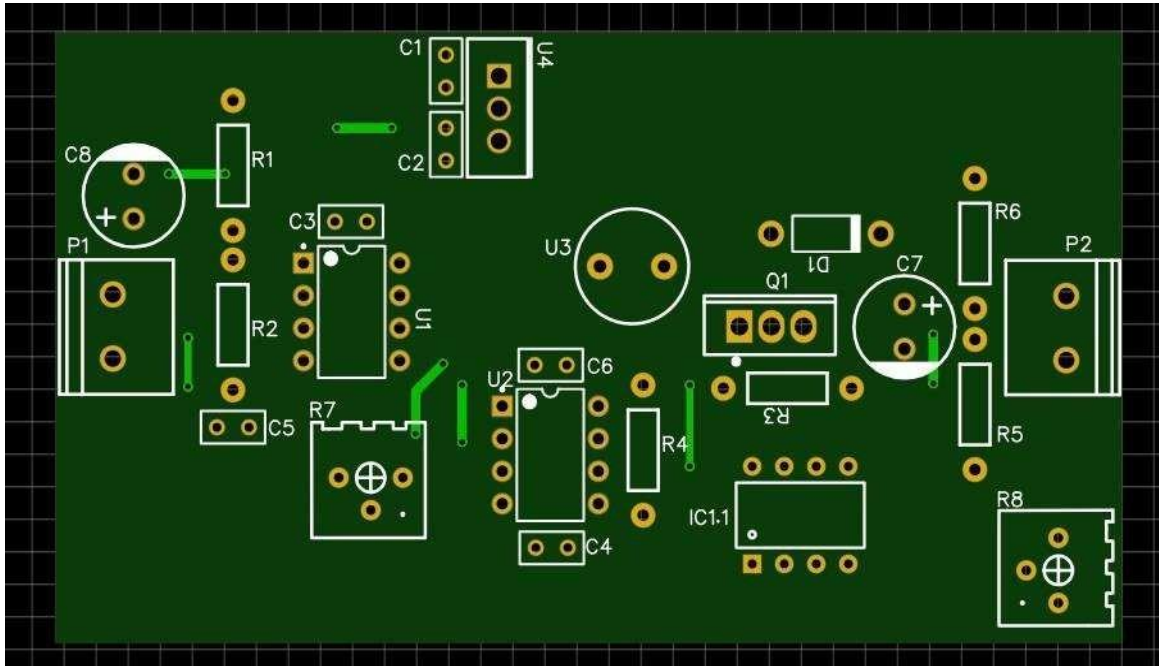


Fig. 4.2.1 Top View Of PCB

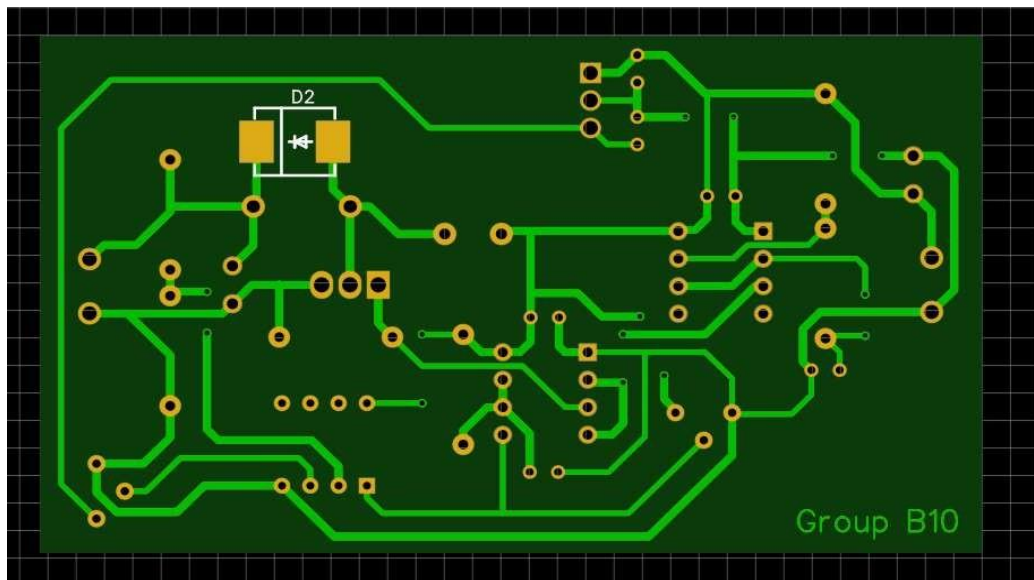


Fig. 4.2.2 Bottom View of PCB

4.3 Flowchart:

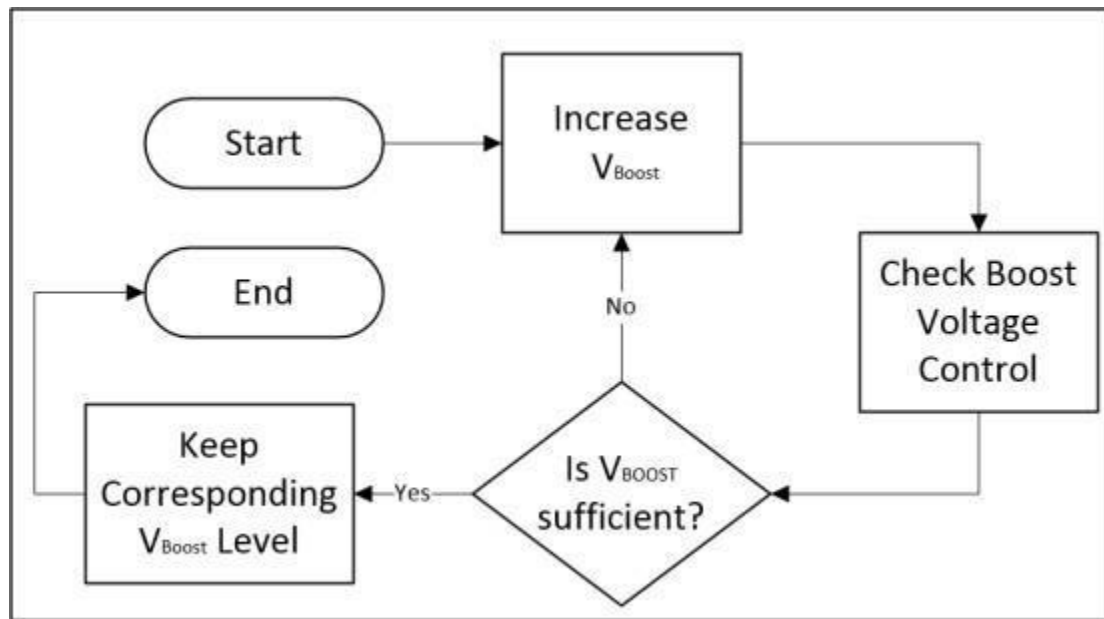


Fig 4.3.1 Flowchart of Working

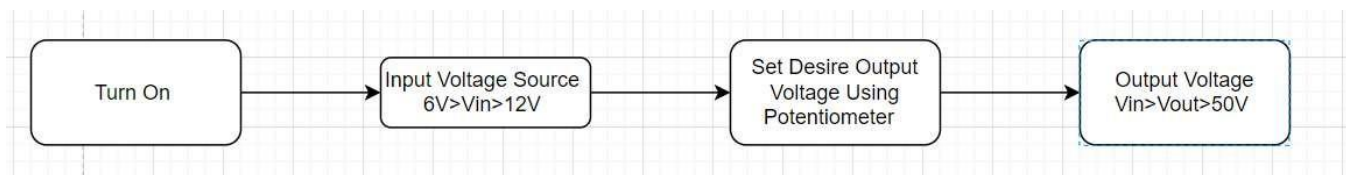


Fig.4.3.2 Flowchart of Process

Chapter 5

Results

This chapter contains the various results obtained during the various stages of the project which includes both the hardware and software results.

The circuit diagram was implemented and simulated using the Proteus software as shown in the given Fig 5.1. This was done to identify any errors present in the connections of the proposed circuit. Any faults present in the circuit were corrected thereafter. In this simulation, when we supply 12V DC input we can get the desired output by changing potentiometer output max till 50V.

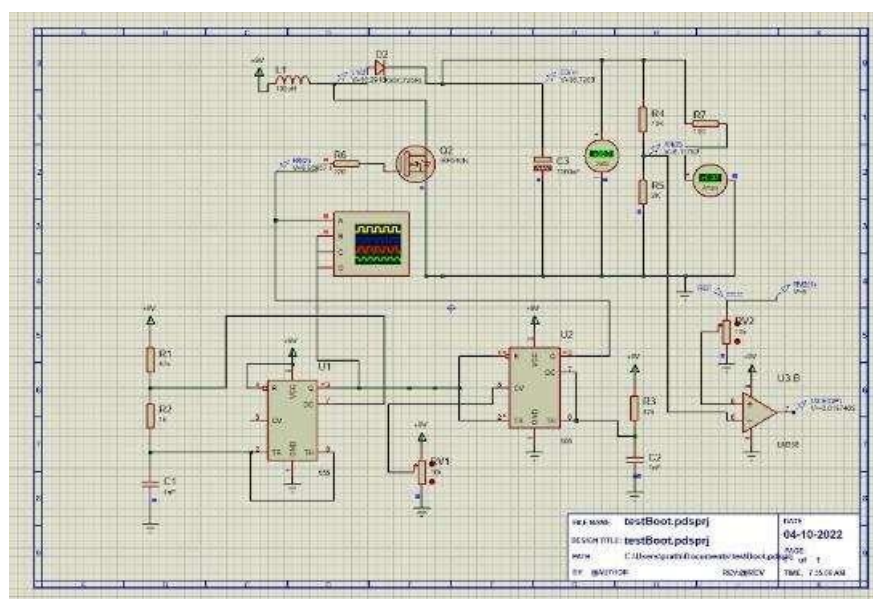


Fig. 5.1 Simulation on Proteus

After successfully checking the circuit on proteus, the next step was physical implementation on the general purpose board. All the components were mounted on GPB to check the proper connection and operation of the ICs on the DSO.

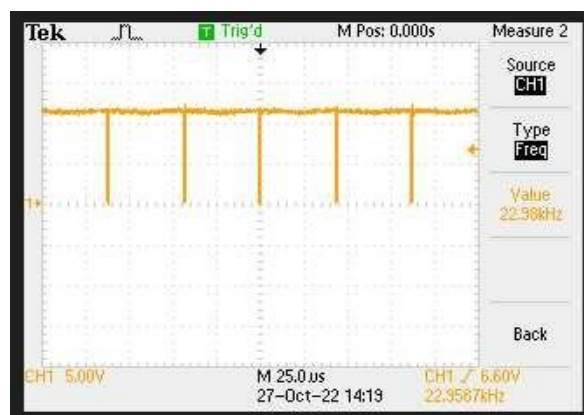


Fig. 5.2 Output waveform of first IC 555

1st IC is in a monostable configuration. Monostable configuration means that the output voltage becomes high for a set duration (T) when a falling edge is detected on pin 2 (trigger). Which is having high duty cycle.


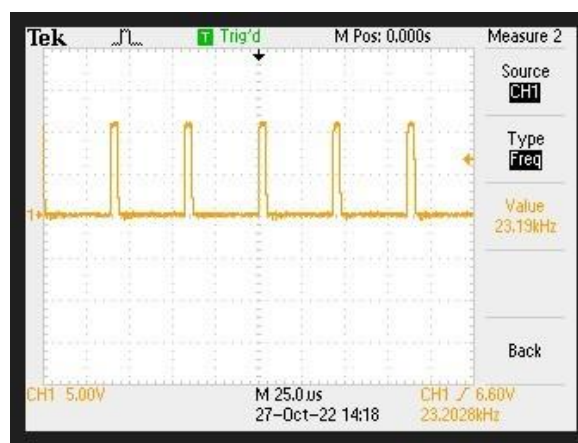


Fig. 5.3 Output waveform of 2nd IC 555

Here the first figure is with a no load output waveform and the second figure is the output waveform of the second IC when the load is attached. Here the duty cycle changes automatically depending on the feedback from (LM358) To Maintain the Output Voltage.

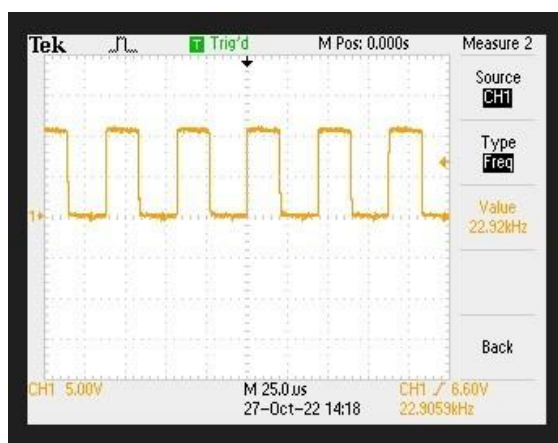

Fig. 5.4 Result on GPB

Input Voltage = 12.19V

Output Voltage= 30.3V

When supply of 12V was supply to the GPB version of the project (*refer to fig 5.4*) the output we get was around 30.3V. And the power efficiency of the circuit exceeds 85%.



Fig. 5.5 Final result on PCB

Input Voltage=12V

Output Voltage= 30.09V

We were getting approximately same result as of GPB version of the project and on the PCB version. Here, also the power efficiency exceeds 85%.

Chapter 7

Conclusion

All of the specifications stated previously have been met by this boost converter design. Simulations using PROTEUS calculated parameters were performed and corresponding waveforms were obtained. The output voltage across the output capacitor is 30V. The power efficiency of the circuit exceeds 85%. However an additional constraint needs to be put on the load. Hardware design of BOOST CONVERTER was done. It is observed, by varying duty cycle output voltage also changes.

References

References:

1. Rosas-Caro JC, Ramirez JM, Peng FZ, Valderrabano A. A DC–DC multilevel boost converter. IET Power Electronics. 2010 Jan 1;3(1):129-37.
2. Nahavandi A, Hagh MT, Sharifian MB, Danyali S. A non isolated multiinput- multioutput DC–DC boost converter for electric vehicle applications. IEEE Transactions on Power Electronics. 2014 May 29;30(4):1818-35.
3. Aghabali I, Bauman J, Kollmeyer PJ, Wang Y, Bilgin B, Emadi A. 800-V electric vehicle powertrains: Review and analysis of benefits, challenges, and future trends. IEEE Transactions on Transportation Electrification. 2020 Dec 15;7(3):927-48.
4. <https://circuitdigest.com/electronic-circuits/a-simple-boost-converter-circuit-using-555-timer-ic>.
5. <https://how2electronics.com/dc-dc-converter-using-555-timer/>
6. <https://www.circuits-diy.com/boost-converter-circuit-using-555-timer-ic/>
7. <https://www.electronicclinic.com/simple-dc-to-dc-converter-using-555-time-ic-6v-to-35-volts-boost-converter/>

Datasheets

NE555: https://www.ti.com/cn/lit/ds/symlink/ne555.pdf?ts=1666974810884&ref_url=https%253A%252F%252Fwww.lcsc.com%252F

LM358: https://datasheet.lcsc.com/lcsc/1811100911_onsemi-LM358DR2G-_C7950.pdf

STPS2045C: [Power Schottky rectifier \(lcsc.com\)](#)

NCE8295A: [Microsoft Word - NCE8295A data sheet.doc \(lcsc.com\)](#)

Voltage Regulator LM7805 5V: [LM340, LM340A and LM7805 Family Wide VIN 1.5-A Fixed Voltage Regulators datasheet \(Rev. L\) \(ti.com\)](#)

SS34: [1912111437_Slkor-SLKORMICRO-Elec--SS34_C408258.pdf \(lcsc.com\)](#)

IRFZ44N: [DATASHEET SEARCH SITE | WWW.ALLDATASHEET.COM \(lcsc.com\)](#)

LM7805: https://www.alldatasheet.com/view.jsp?Searchword=Lm7805%20datasheet&gclid=Cj0KCQjwnvOaBhDTARIsAJf8eVPchHM8aVaRUFURjSzhWI5UxhK5572aCSsb8BzjMLHBHFV-dJwuVC0aAi2rEALw_wcB